

# Transient Voltage Suppressors (TVS) for Automotive Electronic Protection

**SOO MAN (SWEETMAN) KIM**

Vishay Intertechnology, Inc.  
Malvern, Pennsylvania, USA

**A** major challenge in automotive design is protecting electronics – such as control units, sensors, and entertainment systems – against damaging surges, voltage transients, ESD, and noise that are present on the power line. Transient voltage suppressors (TVS) are ideal solutions for automotive electronic protection and have several important parameters for these applications, including power rating, stand-off voltage, breakdown voltage, and maximum breakdown voltage. Following are definitions for these parameters.

## POWER RATING

The power rating of a TVS is its surge-absorbing capability under specific test or application conditions. The industrial-stand-

ard test condition of 10  $\mu$ s/1000  $\mu$ s pulse form (Bellcore 1089 spec. [1]) is shown in Figure 1. This test condition differs from the TVS transient voltage absorbing capability test condition of 8  $\mu$ s/20  $\mu$ s pulse form, as shown in Figure 2.

## BREAKDOWN VOLTAGE ( $V_{BR}$ )

The breakdown voltage is the voltage at which the device goes into avalanche breakdown, and is measured at a specified current on the datasheet.


## MAXIMUM BREAKDOWN VOLTAGE ( $V_C$ : CLAMPING VOLTAGE)


The clamping voltage appears across the TVS at the specified peak pulse current rating. The breakdown voltage of a TVS is measured at a very low current, such as 1 mA or 10 mA, which is different from the actual avalanche voltage in application conditions. Thus, semiconductor manufacturers specify the typical or maximum breakdown voltage in large current.

## STAND-OFF VOLTAGE ( $V_{WM}$ ): WORKING STAND-OFF REVERSE VOLTAGE

The stand-off voltage indicates the maximum voltage of the TVS when not in breakdown, and is an important parameter of protection devices in circuits that do not operate under normal conditions. In automotive applications, some regulation of the automotive electronics is provided by “jump-start protection.” This condition supplies 24  $V_{DC}$  in 10 minutes to 12-V type electronics, and 36  $V_{DC}$  in 10 minutes to

**Figure 1.** Test waveform of TVS (Bellcore 1089). Bellcore 1089 represented the closest approximation to the medium- and high-power conditions encountered by TVS devices at the time when they were developed and proved an easier basis for the range of purposes and applications in which these devices are used than ISO-7637-2 [2] or JASO A-1 [3].

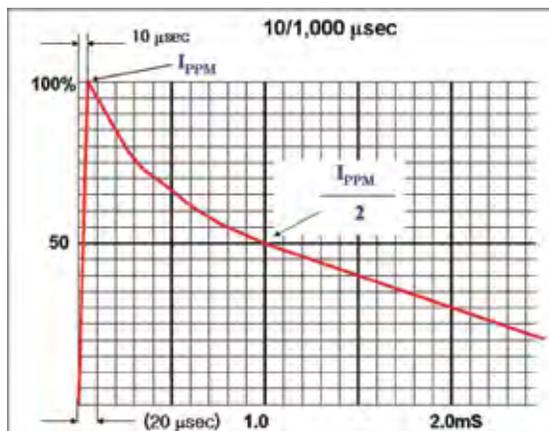

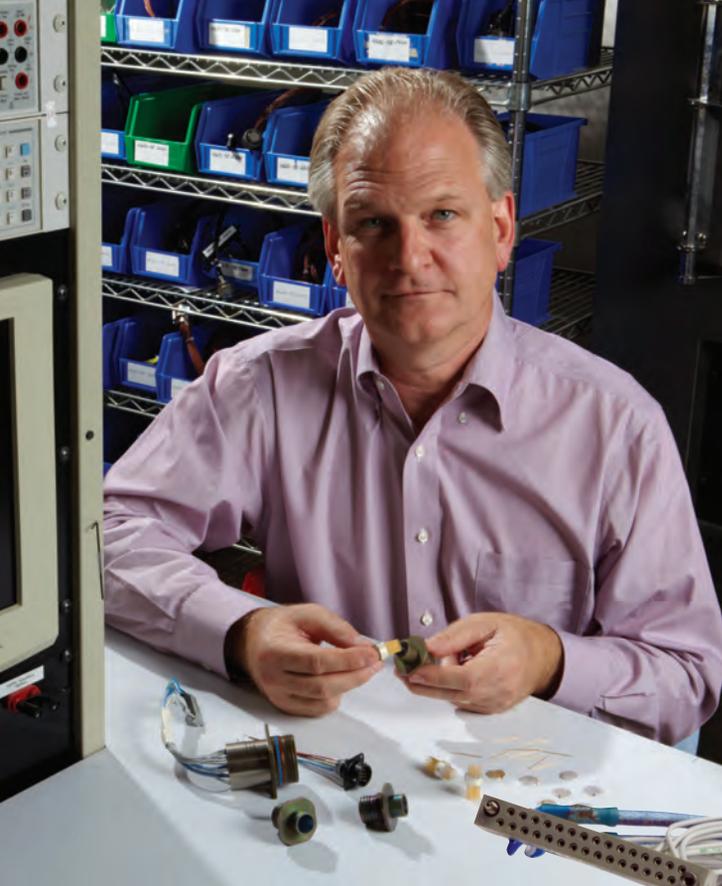

## Our vertical integration gives you custom specialty connectors **FAST!**

“ Our specialty connector team is committed to producing custom EMI filtered and unfiltered connectors with the industry’s shortest lead times. We make our own planar and tubular capacitors, connector shells, shields, seals and grommets. And our expertise in finding the ideal EMI filtering method means you’ll get a higher performing connector, 100% tested for critical electrical parameters. Give me a call to see how we’ll design and build an audio, circular or hermetically sealed connector specifically for your military, commercial or industrial application.”

**Dave Arthurs**  
Product Application Engineer  
Spectrum Advanced  
Specialty Products



Put our  
**innovative** new products  
& **problem-solving**  
expertise to work for you!



Antennas  
& Assemblies



Coaxial Filters  
& Interconnects



Power Filters  
& Film Modules



Specialty Connectors  
& Harnessing



Advanced Ceramics

At the NEW Spectrum Advanced Specialty Products, we’ve expanded our product capability to include a wider range of sophisticated components and assemblies. Our engineering teams continue to provide custom application-specific solutions exceeding our customer’s mechanical, electrical and power requirements. The Spectrum design process begins with our extensive library of standard components, which we frequently develop into custom assemblies offering you a more complete, high performance solution... saving you time and money.

**See how our expertise can work for you,  
call 888.267.1195 or visit [SpecEMC.com](http://SpecEMC.com)**




Check out our  
**NEW Specialty  
Connector Video @  
[SpecEMC.com/specvid](http://SpecEMC.com/specvid)**



**SPECTRUM**  
Advanced Specialty  
PRODUCTS

part of  
**api**   
technologies corp.


## surge & transients

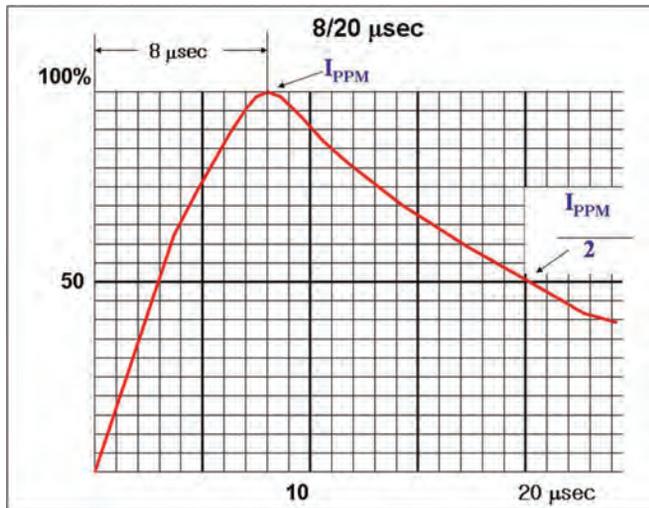


**Figure 2.** Test waveform of TVS. ESD protection devices are traditionally tested and specified for their ability to absorb an 8 μs/20 μs surge pulse since this allows better differentiation between the abilities of various devices than the IEC61000-4-2 pulse test, which all devices should be able to pass regardless of their stated ESD capability.

24-V type electronics without damage or malfunction of the circuit. Thus, the stand-off voltage is one of the key parameters in TVS for automotive electronics.

## TRANSIENT VOLTAGE SUPPRESSORS FOR AUTOMOTIVE ELECTRONIC PROTECTION

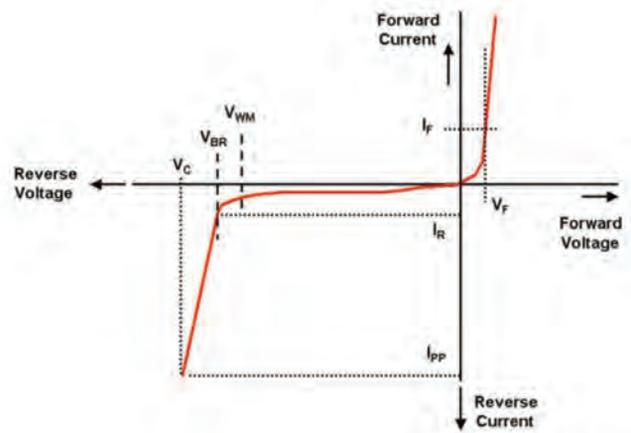

**Figure 3.** Parameters of voltage and current.

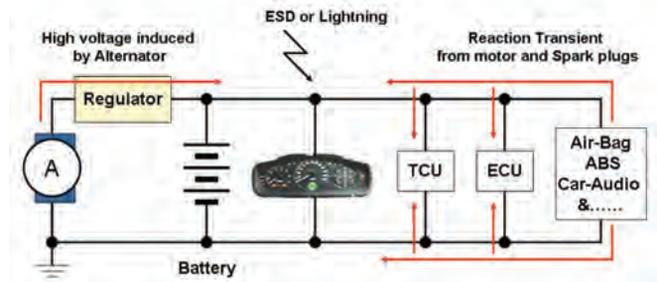

**Figure 4.** Typical vehicle power bus.

### Curtis Industries/Filter Networks

#### INNOVATIVE ENGINEERING SOLUTIONS

Outstanding Performance and Selection on RFI Power Line Filters and Terminal Blocks.

#### Filters

- GENERAL PURPOSE FILTERS
- 3-PHASE
- AC AND DC FILTERS
- CUSTOM FILTERS
- MILITARY FILTERS

#### Terminal Blocks

- BARRIER STYLE
- PCB MOUNT
- DIN RAIL MOUNTED
- CUSTOM MOLDING



Our engineering and sales departments are ready to address your filtering needs with results that are PROFESSIONAL - QUICK - ECONOMICAL - QUIET.

For product information contact:

**Curtis Industries/Filter Networks**  
2400 S. 43rd Street  
Milwaukee, WI 53219

tel: 414-649-4200 or 1-800-657-0853

[www.curtisind.com](http://www.curtisind.com) [cisales@curtisind.com](mailto:cisales@curtisind.com)  
[www.filternetworks.com](http://www.filternetworks.com)



**Curtis Industries**  
A Div. of Powers Holdings, Inc.

**FILTER NETWORKS**  
A Curtis Industries Company

ISO 9001 Registered

Tri-Mag, Inc. can build standard and custom design EMI filters for any industry:

### MEDICAL, MILITARY & INDUSTRIAL

EMI FILTERS Single-Phase Filters • Three-Phase filters • Power Entry Modules • IEC Inlet Filters



**Military**



**Medical**



**Medical**



**Industrial**

In addition to our wide range of standard products and our capabilities of building custom products to fit any application, all of **Tri-Mag, Inc.** Filters are built in the **USA**.

**ROHS Compliance**

**TRI-MAG, Inc.**  
your **POWER Specialists**

1601 N. Clancy Ct. Visalia, CA 93291 • Phone: (559) 651-2222 • Fax: (559) 651-0188  
[www.tri-mag.com](http://www.tri-mag.com) • [sales@tri-mag.com](mailto:sales@tri-mag.com)

# Your connector can be an EMI filter, too!

Quick, easy,  
permanent  
retrofit with  
EESeal®  
FilterSeals

Installs in seconds, no soldering,  
just push in

Durable, conformal  
elastomeric body

Meets wide barrage of  
mil-standard tests

Pin-to-pin & pin-to-shell capacitors,  
MOVs, resistors, shorts, etc.

AS9100 Certified



Custom designs to  
you in just days!

Call for a free sample.



505.243.1423 • [www.eeseal.com](http://www.eeseal.com)

U.S. Patent Nos. 5,686,697 and 6,613,979, Canadian Patent No. 2,209,660, and European Patent No. 0 801 815 • © 2011 Quell Corporation



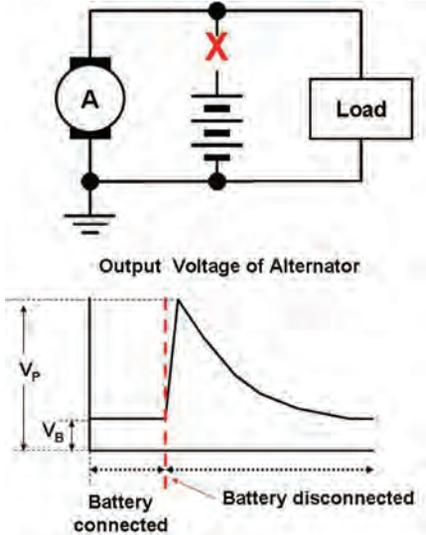


Figure 5. (right) Output voltage of alternator in load dump condition.

**PRIMARY PROTECTION OF THE AUTOMOTIVE POWER LINE (LOAD DUMP)**

Automotive electronics, such as electronic control units, sensors, and en-

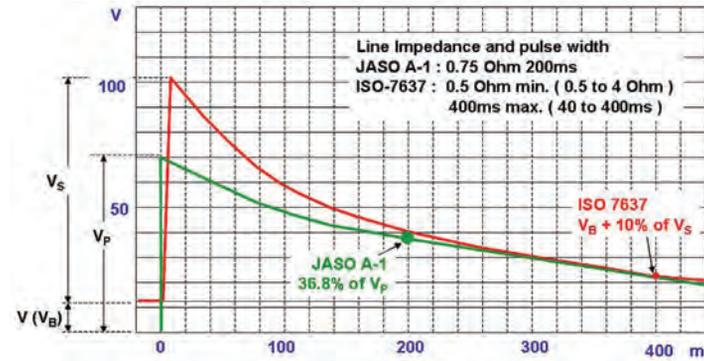


Figure 6. For ISO-7637-2 test conditions, the standard condition is a VS range of 65 V to 87 V, and Ri (line impedance) range of 0.5Ω to 4Ω.

tertainment systems, are connected to one power line. The power sources for these electronics are the battery and alternator, both of which have unstable output voltages that are subject to temperature, operating status, and other conditions. Additionally, ESD, spike noise, and several kinds of transient and surge voltages are introduced into the power and signal line from automotive systems that use solenoid loads, such as fuel injection, valve, motor,

electrical, and hydrolytic controllers.

**WHAT IS LOAD DUMP?**

The worst instances of surge voltage are generated when the battery is disconnected when the engine is in operation, and the alternator is supplying current to the power line of the vehicle. This condition is known as “load dump,” and most vehicle manufacturers and industry associations specify a maximum voltage, line impedance, and time duration for this load dump status, as shown in Figure 5. The source impedance for load dump is higher than for the normal transient tests because the battery is disconnected and only the alternator, whose internal coil acts like a current limit resistor, is sourcing the power.

The following general considerations of the dynamic behavior of alternators during load dump apply:

- a) The internal resistance of an alternator, in the case of load dump, is mainly a function of alternator rotational speed and excitation current.
- b) The internal resistance  $R_i$  of the load dump test pulse generator shall be obtained from the following relationship:

$$R_i = ( 10 X U_{nom} X N_{act} ) / ( 0.8 X I_{rated} X 12,000 \text{ min}^{-1} ),$$

where

$U_{nom}$  is the specified voltage of the alternator;

$N_{act}$  is the specified current at an alternator speed of  $6,000 \text{ min}^{-1}$  (as given in ISO 8854);

$I_{rated}$  is the actual alternator speed, in reciprocal minutes.

Two well-known tests simulate this condition: the U.S.’s ISO-7637-2 Pulse 5 and Japan’s JASO A-1 for 14-V powertrains and JASO D-1 for 27-V

**Your Signal Solution®**

Since 1952 we have provided ferrites for your signal solutions. We are committed to developing with you as technology advances and needs change for EMI Suppression, Power, and RFID Antenna Applications.

Fair-Rite places the highest value on quality, engineering, and service. Our experienced team of engineers can assist with new designs and technical support.

**Fair-Rite Products Corp.**  
www.fair-rite.com

P.O. Box 288, 1 Commercial Row, Wallkill, NY 12589-0288 USA  
Phone: 1-888-FAIRRITE (324-7748)/845-895-2055 • Fax: 1-888-FERRITE (337-7483)/845-895-2629  
E-mail: ferrites@fair-rite.com

ISO 9001 CERTIFIED TS 16949 REGISTERED

	V TOTAL (V <sub>p</sub> ) (V)	V <sub>s</sub> V	V <sub>A</sub> V	R <sub>i</sub> (Ω)	TIME (ms)	CYCLE TIME
JASO A-1	70		12.0	0.8	200	1
	88		12.0	1.0	200	1
ISO 7637-2 Pulse 5	78.5 to 100.5	65 to 87	13.5	0.5 to 4.0	400	1

Table 1. Major load dump test conditions for 14-V powertrains.

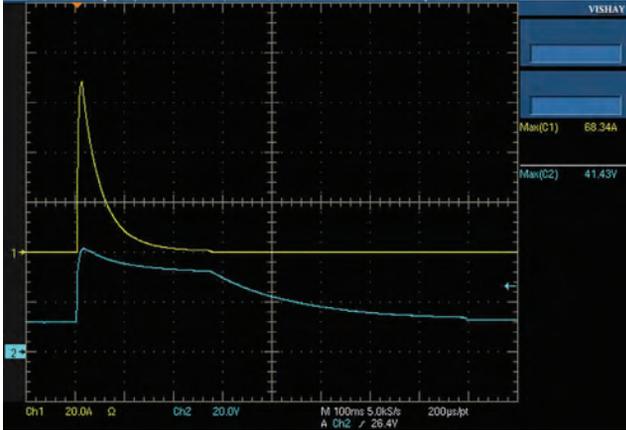


Figure 7a. Clamped voltage and current of SM5S24A in ISO 7637-2 test.

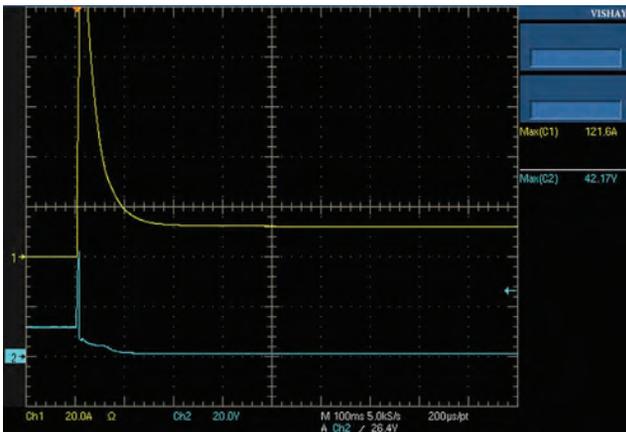


Figure 7b. Clamped voltage and current of load dump TVS failures in ISO7637-2 test.

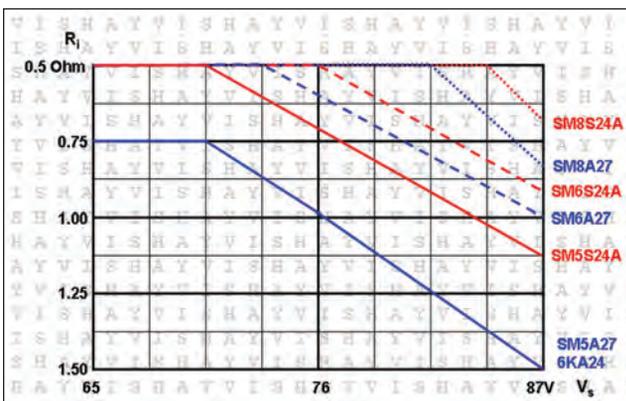


Figure 7c. Maximum clamping capability of Vishay load dump TVS in ISO7637-2 test.

powertrains. In this section we review the application of TVS for load dump in 14-V powertrains.

### SPECIFICATION AND RESULTS OF LOAD DUMP TESTS

The U.S.'s ISO-7637-2 Pulse 5 and Japan's JASO A-1 tests for 14-V powertrains are simulated in Table 1.

Some vehicle manufacturers apply different conditions for the load dump test based on ISO-7637-2 Pulse 5. The peak clamped current of the load dump TVS will be estimated by the following equation:

Calculation for peak clamping current

$$I_{PP} = (V_{in} - V_C) / R_i$$

$I_{PP}$ : Peak clamping current

$V_{in}$ : Input voltage

$V_C$ : Clamping voltage

$R_i$ : Line impedance

The current and voltage waveforms of Vishay's SM5S24A

## TECH-NOVATION to the Market

TOTAL EMI SOLUTION PROVIDER  
*EMI Problems? We've got Solutions!*

Absorbing EMI Noise



**ABSORBER SHEETS**

FERRITE SHEET  
FFS FERRITES



**NEW!**

EMI WINDOW  
SHIELDING FILM



Transparent  
Low Resistance

Excellent Conductivity  
in X, Y and Z axes



**NEW!**

**EZ-Foam**

SMT  
GROUNDING  
CONTACTS



Board Level  
EMI solution

THERMAL PADS



EMI + Thermal  
Dual Function

EMI Shielding Materials + Ferrite Cores



EMI GASKETS


EMI TAPES



FERRITES

FERRITES TILES  
FOR ANECHOIC CHAMBERS



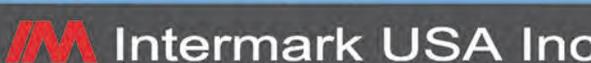

**Intermark USA Inc**  
www.intermark-usa.com  
ph. 408-971-2055 fx. 408-971-6033

EMI Solutions • RoHS Compliance 

in the ISO-7637-2 test of 87V Vs, 13.5V V<sub>batt.</sub>, 0.75 Ohm Ri and 400ms pulse width as shown in Figure 7A.

In Figure 7B the clamped voltage and current of load dump TVS fail in the ISO-7637-2 test of 87V Vs, 13.5V V<sub>batt.</sub>, 0.5 Ohm Ri and 400ms pulse width because the device was over-dissipated. The clamping voltage drops to near zero, and the current passed through the device is increased to the maximum allowed by the line impedance.

The maximum clamping capability of Vishay load dump TVS of ISO-7637-2 pulse 5 test condition with 13.5V V<sub>batt.</sub>

and 400ms pulse width is shown in Figure 7C. To prevent failure, such as that shown in Figure 7B, it is important to respect the maximum rating of the TVS.

**PROTECTION AGAINST NEGATIVE-GOING TRANSIENTS AND REVERSED SUPPLY VOLTAGE**

There are two kinds of load dump TVS for the primary protection of automotive electronics: epitaxial and non-epitaxial. Both product groups have similar operating breakdown characteristics in reverse bias mode. The difference is that epitaxial

TVSs have low forward voltage drop (VF) characteristics in forward mode, and non-epitaxial TVSs have relatively high VF under the same conditions. This characteristic is important to the reverse voltage supplied to the power line. Most CMOS ICs and LSIs have very poor reverse voltage capabilities.

The gates of MOSFETs are also weak in reverse voltage, at - 1 V or lower. In the reversed power input mode, the voltage of the power line is the same as the voltage of the TVS VF. This reverse bias mode causes electronic circuit failure. The low forward voltage drop of EPI PAR TVSs is a good solution to this problem. Another method to protect circuits from reversed power input is utilizing a polarity protection rectifier into the power line, as shown in Figure 8. A polarity protection rectifier should have sufficient forward current ratings, and forward surge and reverse voltage capabilities.

**SECONDARY PROTECTION OF THE AUTOMOTIVE POWER LINE**

The primary target of protection circuits in automotive systems is high surge voltages, but the clamped voltage is still high. Secondary protection is especially important in 24- V powertrains, such as found in trucks and vans. The main reason for this is the maximum input voltages for most regulators and dc-to-dc converter ICs for automotive applications are 45 V to 60 V. For this kind of application, using secondary protection, as shown in Figure 9, is recommended.

Adding resistor R onto the power line reduces the transient current, allowing smaller power-rating TVSs as the secondary protection. Current requirements for microprocessor and logic circuits in electronic units are

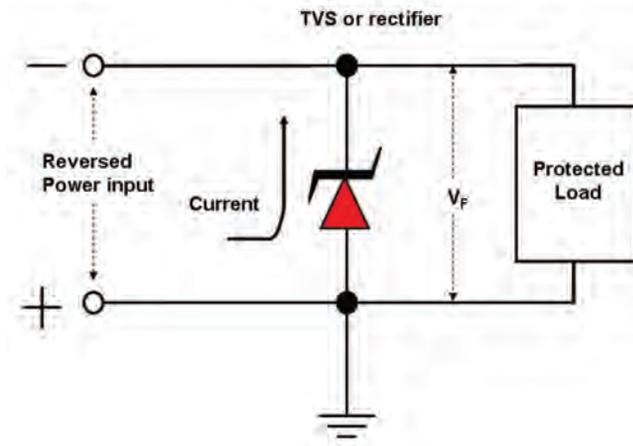


Figure 8. Reverse bias status.

150 mA to 300 mA, and the minimum output voltage of a 12-V battery is 7.2 V at -18°C, or 14.4 V for a 24-V battery under the same conditions. In a 24-V battery under the above conditions, the supply voltage at a 300-mA load is 8.4 V at R = 20 Ω, and 11.4 V at R = 10 Ω at a minimum voltage of 14.4 V (24-V battery voltage in - 18 °C).

$$V_L = (V_{min} / (V_{min} / I_L)) \times ((V_{min} / I_L) - R)$$

$V_L$ : Voltage to load

$V_{min}$ : Minimum input voltage

$I_L$ : Load current

$R$ : Resistor value

Power rating of R =  $I^2R$

This supply voltage is higher than the minimum input voltages for most voltage regulators and DC/DC converter ICs to avoid wrong operation of circuit by low voltage input.

While safety and reliability issues are important considerations in automotive systems, they are beyond the scope of this article.

**CONCLUSION**

In this article, we've described all the transients and their modes that can damage automotive electronic systems. We've gone on to discuss the important parameters of TVSs, and have demonstrated that with the appropriate specifications, these devices can protect circuits against all transients and the load dump condition.

**REFERENCES**

- [1] Bellcore 1089, <https://www.scte.org>
- [2] ISO/DIS-7637-2.3 2004 Road vehicles – Electrical disturbances from conduction and coupling – Part 2. Electrical transient conduction along supply lines only. [www.iso.ch](http://www.iso.ch)
- [3] JASO D 001-94 Japanese Automobile standard, <http://www.jsae.or.jp>
- [4] ES-XW7T-1A278 - AC Component and Subsystem Electromagnetic Compatibility, Worldwide Requirements and Test Procedures, Ford Motor Company, <http://www.fordemc.com>


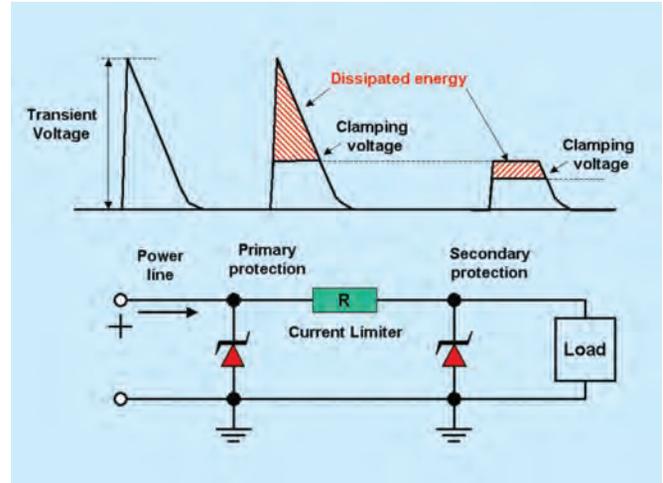


Figure 9. Secondary protection circuit.

- [5] IEC 61000-4-5 International Standard Electromagnetic Compatibility (EMC) – Part 4-5: Testing and measurement techniques, surge immunity test. [www.iec.ch](http://www.iec.ch)

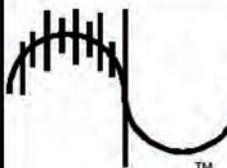SOO MAN (SWEETMAN) KIM studied electronic engineering at YoungNam University in Korea and has worked for Vishay General Semiconductor on field application engineering and product marketing applications for rectifier and TVS devices since 1987. ■



**EMI  
FILTER  
COMPANY**

Artful  
Craftsmanship,  
Superior  
Service



Low pass  
EMI Filters  
to suit your  
application

An ISO 9001:2008 Company  
12750 59th Way North  
Clearwater, FL, 33760  
Sales@emifiltercompany.com  
1-800-323-7990