



Phototriac Basics

By Deniz Görk and Achim M. Kruck

INTRODUCTION

Phototriacs have traditionally been used as solid-state AC switches. In many industries such as industrial and process control, it is not uncommon to use the term solid-state relay optotriac and phototriac synonymously.

Vishay has a wide range of phototriacs which span the gamut in terms of performance, features, and cost. Vishay's phototriacs vary, in terms of break-down voltage, power rating, and a parameter which is most important when designing with phototriacs and TRIACs in general, the dv/dt parameter. Most of the applications for phototriacs involve their use as AC switches or as driver for a power TRIAC, however, they can also be used as simple DC latches.

Phototriacs are used where electrical isolation is required from driving source to load. This isolation requirement can be driven by electrical safety as well as other requirements like ground-loop breaking, EMI and RFI mitigation, etc.. All Vishay couplers meet UL safety agency standards and meet VDE requirements when ordered with VDE option.

INPUT (EMITTER SIDE)

Vishay's phototriacs are driven by a GaAs LED, which generates optical energy that is collected by a photoSCR. Similar to standard optocoupler products it is important to perform a worst case analysis, when determining the optimum driving current I_{FT} under worst case temperature and component variance conditions.

The first thing to determine is the required turn-on time for the switch in question. The faster the desired turn-on time, the more current is required to turn on the device. Fig. 1 is a graphical presentation of this parametric behavior. It clearly demonstrates two important trends: Trigger delay increases with increasing temperature and decreasing I_{FT} .

In addition to the effects of temperature and switching time, one needs to take into account the power dissipated in the optocoupler as a whole and the LED and the phototriac output in particular. When attempting to calculate the maximum permissible LED current, it is important to determine the forward voltage drop across the LED which is illustrated in Fig. 2, with Fig. 3 providing the maximum allowable power dissipation as a function of ambient temperature.

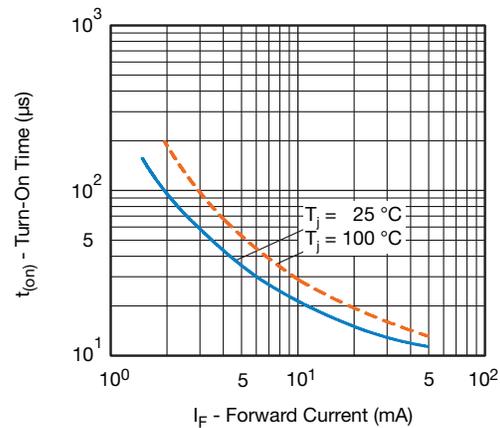


Fig. 1 - Turn-On Time vs. Forward Current

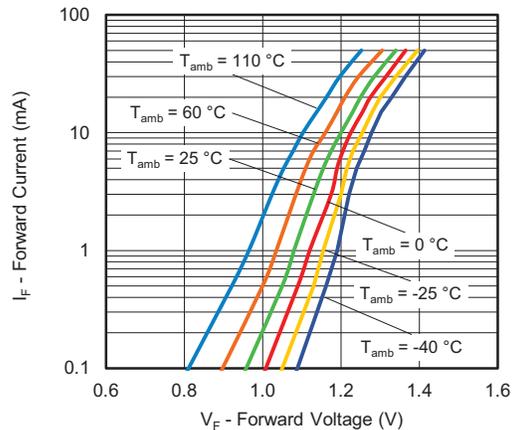


Fig. 2 - Forward Current vs. Forward Voltage

Phototriac Basics

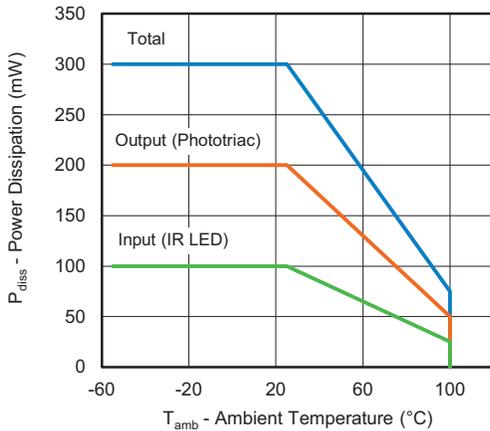


Fig. 3 - Power Dissipation vs. Ambient Temperature

Finally, when discussing LED drive design it is important to take the LED aging into account. It is a matter of fact that GaAs LEDs degrade over time; however, the amount of degradation is usually not something that limits the performance of most end-products given normal operating conditions and equipment life cycles.

The parameters that affect LED aging are temperature and LED drive current. As the temperature and LED current increase the aging process of the LED also increases. This process is only significant under the most extreme examples of temperature and current.

OUTPUT (DETECTOR SIDE)

A TRIAC is a subset of a family of semiconductors referred to as thyristors. These are all four-layer bipolar devices with various triggering configurations. Regardless of the specific flavor of thyristor used, they all are built on the basic thyristor structure illustrated below in Fig. 4.

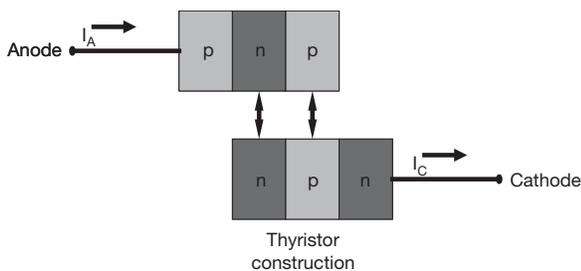


Fig. 4 - Thyristor Construction

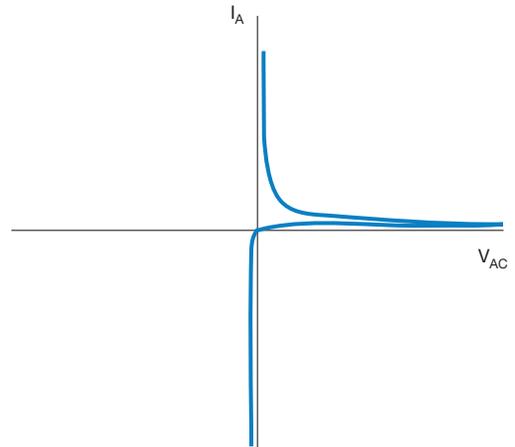


Fig. 5 - IV Curve

Fig. 5 is the IV curve most commonly associated with thyristor components. Note that the curve of a thyristor is actually quite similar to the characteristic curve of a standard diode, with the exception that the current increases slowly with voltage until a maximum point - commonly known as the “snapback” voltage - is reached. Having reached this point, the voltage across the thyristor drops sharply and the current begins to increase in a highly exponential function, as would be expected in a standard diode.

Fig. 5 illustrates this behavior using a “typical” curve for a classic silicon controlled rectifier (SCR).

The functionality of a thyristor can be easily understood if one thinks of the device as two bipolar transistors where the collector of one transistor drives the base of the other, as illustrated in Fig. 6. Thus, when this device is turned on it will remain on until the current through the device drops to zero. This is a simplified view of TRIAC performance and ignores some second-order effects that are key to successful TRIAC designs.

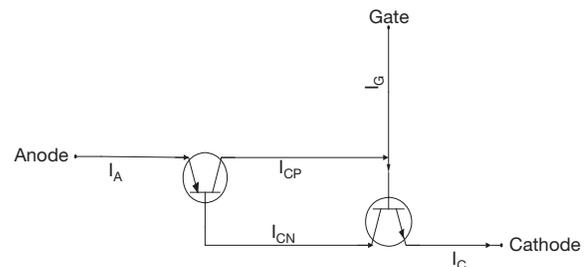


Fig. 6 - TRIAC Circuit

Phototriac Basics

A thyristor can be triggered by applying a voltage across its output terminals of sufficient amplitude to exceed its breakdown or snapback voltage. This type of triggering method is quite common and is used in thyristor devices referred to as DIACs; however, conduction can also be achieved in a more controllable fashion by connecting a triggering gate that allows for the injection of minority carriers into the gate region. In this way, a TRIAC can be triggered in much the same way as a bipolar transistor. This type of thyristor configuration is known as an SCR (silicon controlled rectifier). Its schematic symbol and internal construction are illustrated in Fig. 7.

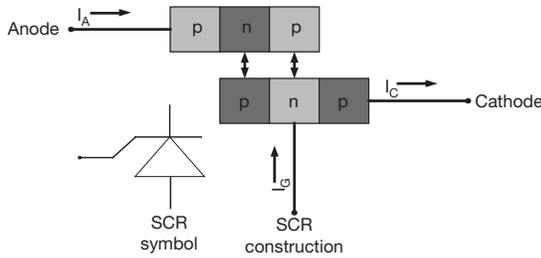


Fig. 7 - SCR Construction

Such devices act as uni-directional AC switch. Uni-directional, because current is allowed to flow in only one direction and AC switch, because it relies on the zero current crossing of the AC waveform to turn off the switch, once it has been triggered. The final configuration that needs to be considered is the TRIAC, which is a bi-directional AC switch. If one understands the characteristics and functionality of an SCR, a TRIAC can be thought of as two back-to-back SCRs with a common gate. This structure allows current to flow in both polarities and thereby constitutes a highly effective AC switch. Fig. 8 illustrates the schematic symbol and the IV characteristic curves of a typical TRIAC. Note that the snapback voltage decreases as the gate current increases from an initial zero point value.

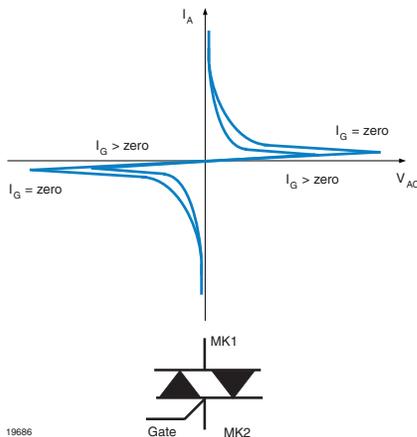


Fig. 8 - TRIAC

Finally, a phototriac can be implemented in two different ways, with the main differentiation being on the detector portion of the device. In one case the TRIAC itself can be designed such that it has a photosensitive gate region, in a way analogous to the base region of a phototransistor. This is the preferred detector configuration for inexpensive devices. Higher-performing devices employ a detector configuration similar to the one illustrated in Fig. 9. This detector configuration does not employ a simple TRIAC with a photosensitive region; its more sophisticated and complex approach consists of a power stage made up of a TRIAC, or two SCRs driven by a driver stage, which is in turn triggered by a photosensitive device such as a photodiode or phototransistor. This approach has the advantage of giving the designer the flexibility of adding circuitry to the driver stage to increase parametric performance. Moreover, the physical separation of the power stage from the driver and trigger sections of the device has an inherent benefit in terms of noise immunity. The physical isolation of the separate stages of the device decreases coupling due to parasitic impedances between the output circuit and the drive and trigger circuitry.

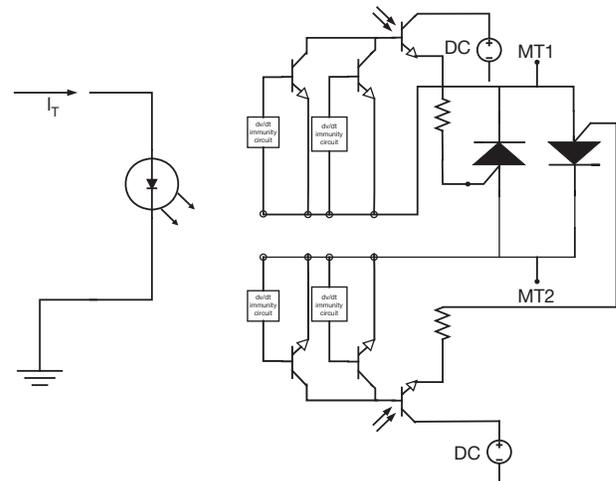


Fig. 9 - Phototriac Functional Diagram

TYPES OF PHOTOTRIACS

There are two different types of phototriacs available, non-zero crossing (NZC) and zero crossing (ZC) phototriacs, each of which are suitable for different applications. Vishay offers both non-zero crossing and zero crossing phototriacs to be able to provide a solution for all different applications.

Phototriac Basics

NON-ZERO CROSSING PHOTOTRIAC (NZC)

The NZC phototriacs are used for the application that requires a fine and phase angle independent control. Example of such application is light dimmers where the light brightness is dependent on when in a half wave the phototriac has been switched on and finally determines the amount of switched power. Another example for NZC phototriac application is motor control where fine control would cause smooth and uninterrupted movements.

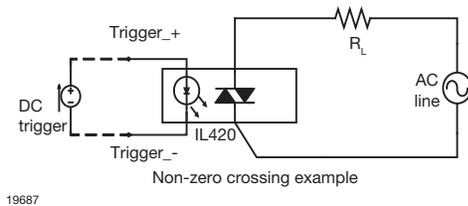
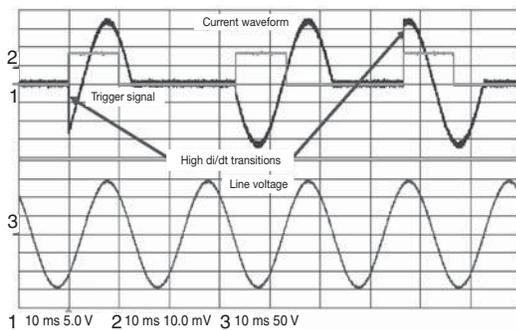


Fig. 10 - NZC TRIAC Waveforms

Randomly switching NZC phototriacs, can produce sharp di/dt transients across the TRIAC, resulting in electromagnetic interferences (EMI) or radio frequency interferences (RFI).

Today, in most product designs, controlling the EMI and RFI compliance is of increasing concern. The sharp frequency generated by the sharp di/dt transitions make themselves known by radiating directly out into space as RFI and by operating down the power lines which in turn also radiate the lower frequency harmonics that would not otherwise be radiated directly.

ZERO CROSSING PHOTOTRIAC

ZC phototriacs are limited to applications where the control time constant is significantly large. Such applications are heater control or solenoid drivers.

There are several advantages to use of the ZC phototriacs. Fig. 11 is an example of ZC phototriac application.

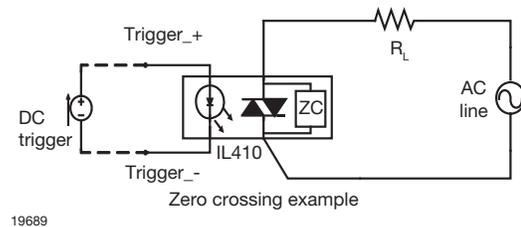
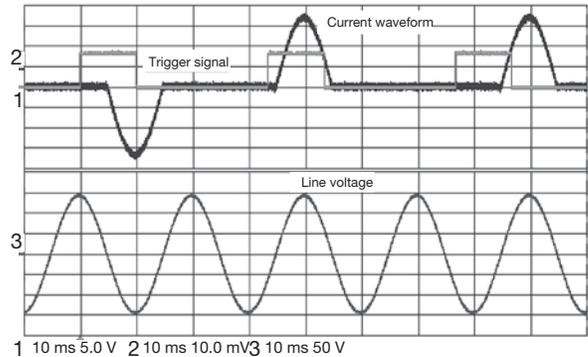


Fig. 11 - ZC TRIAC Waveforms

The reduction of RFI is often the critical reason for using a ZC phototriac. It is a known fact that any signal which is not a sinusoidal function is made up of a fundamental frequency and an infinite series of harmonics of decreasing amplitude. The higher the frequency of the harmonics generated, the easier it is to effectively propagate it into free space with an antenna of small dimensions. Hence, if you do not want to generate noise, make your waveforms as close to sinusoidal waveforms as possible. Fig. 12 graphically illustrates this point.

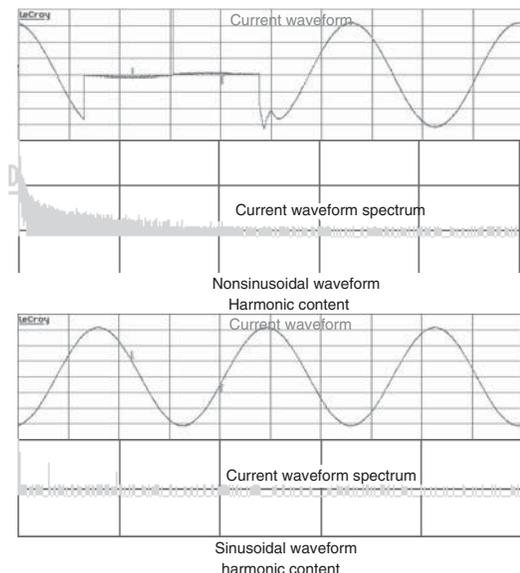


Fig. 12 - Harmonic Content of Non-Sinusoidal Current Waveforms

Phototriac Basics

Another advantage of a zero-voltage triggering phototriac is the fact that since the trigger always occurs at the zero crossing point, it allows the maximum amount of time for current to build up across an inductive load. This is illustrated by the fundamental equation:

$$V = L \times di/dt$$

and the waveforms in Fig. 13 and Fig. 14.

In Fig. 13, a motor contactor was first triggered with a NZC TRIAC, with the result that there was not enough time for current to build up to a sufficient magnitude to activate the contactor armature. In Fig. 14, current was given the full half cycle, resulting in a larger peak current build up, and thus contactor closure.

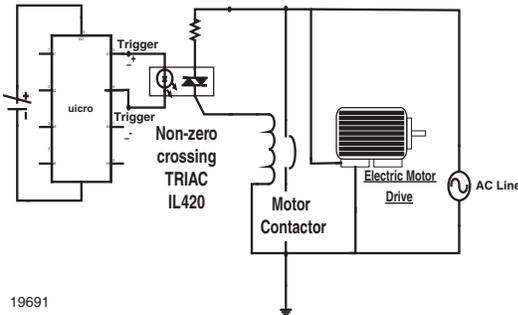
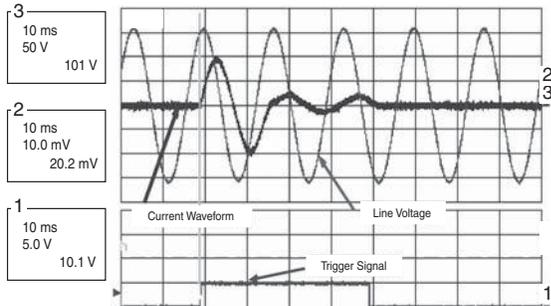


Fig. 13 - NZC TRIAC - Lower Peak I

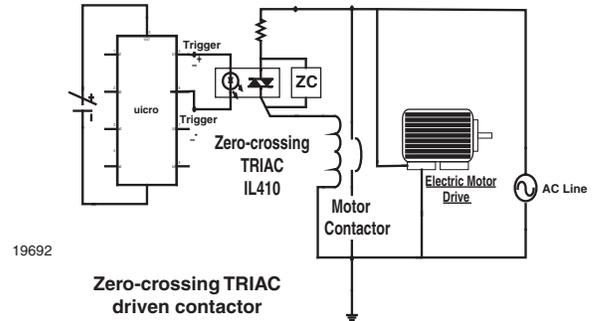
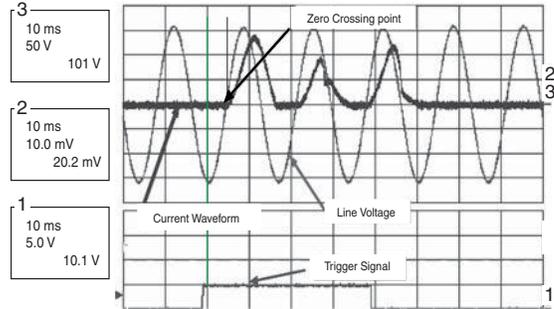


Fig. 14 - ZC TRIAC - Higher Peak I

A zero-crossing implementation does not necessarily mandate the use of a ZC phototriac. A zero-crossing detector can be implemented using various approaches ranging from IC comparators and op amp circuits to simple discrete devices. When one takes into account the increase in circuit complexity, added component cost, and the requirement for galvanic isolation between the TRIAC output and input driving LED, and the need to reduce board real estate, a ZC phototriac looks very attractive as illustrated in the two schematics of Fig. 15 and Fig. 16.


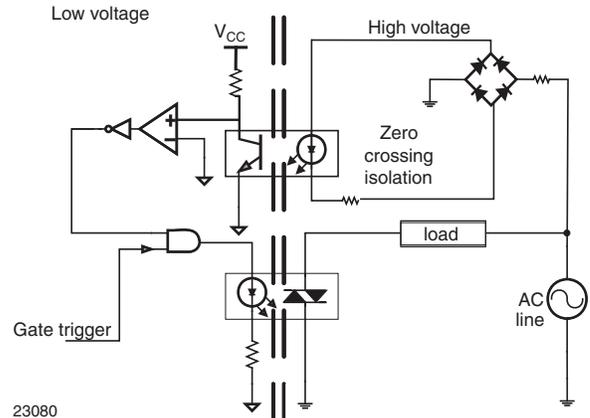


Fig. 15 - Discrete ZC Solution

Phototriac Basics

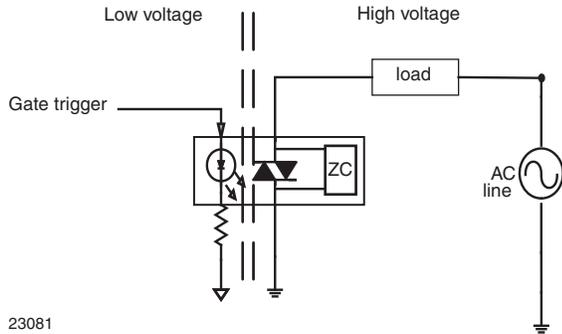

23081

Fig. 16 - ZC TRIAC Solution


PHOTOTRIAC AS STATIC SWITCHES

Thyristors have been around longer than any other type of power semiconductor, and for many years they ruled the domain of solid-state power switching exclusively. Today, with the advances in power MOSFET technology, TRIACs are sometimes replaced by MOSFETs. Yet when it comes to low-cost AC switching applications, TRIACs still have a very important role.

In many applications, TRIACs are used instead of a simple mechanical switch because of the following advantages:


1. Solid-state reliability
2. Elimination of contact bounce
3. Elimination of contact arcing
4. Small size to current handling capacity

Fig. 17 illustrates what is arguably the simplest TRIAC switch imaginable. It provides all of the advantages listed above.

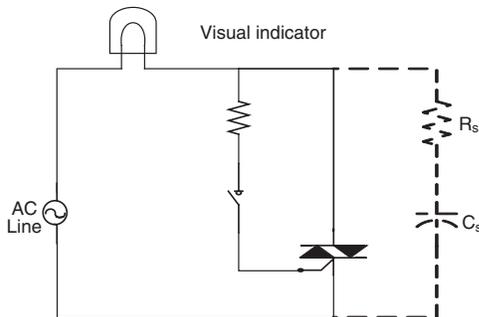

23082

Fig. 17 - Simple Static Switch Application

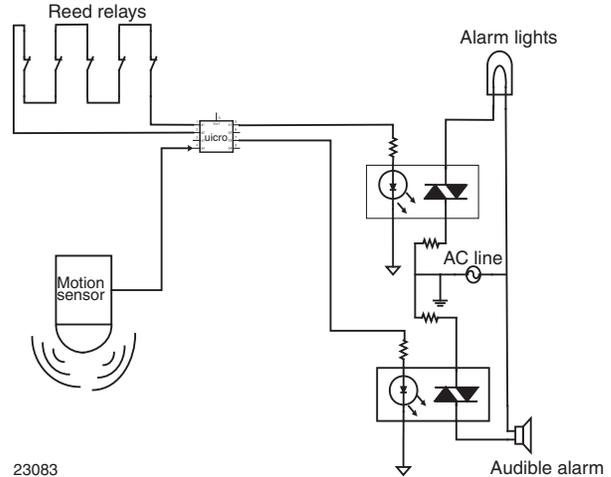

23083

Fig. 18 - Alarm Switch Application

Replacing the TRIAC with a phototriac would provide the further advantage of safety isolation from the high-voltage output to the triggering switch. This is of vital importance if the low-voltage triggering circuit is accessible to the operator or devices are susceptible to noise. This type of application refinement is illustrated in Fig. 18.

TRIACs, as static switches, are commonly used on the output of power supplies as “crowbar” protection. This TRIAC solution is illustrated in Fig. 19. Here the TRIAC is used as a DC latch rather than in its conventional role as an AC switch. It works like any other type of overvoltage sensing scheme. A comparator senses the output voltage and triggers an alarm based on some predetermined trip point. A crowbar circuit has the added feature of tying a power TRIAC across the output of the supply and having this TRIAC triggered by the output voltage comparator circuit. Consequently, when the TRIAC is triggered into its conduction mode by an overvoltage condition, it latches into a conduction mode, due to the fact that the TRIAC will not turn off until a zero current crossing turns off the TRIAC. Thus, the crowbar overvoltage protection scheme protects any output load from any possible overvoltage condition by forcing the output low by “shorting” the output.

Phototriac Basics

PHOTOTRIAC BASED SOLID-STATE RELAYS

Solid-state relays (SSRs) were once the exclusive realm of thyristor devices, but since the advent of power MOSFETs this is no longer the case. Today thyristors still comprise a large share of the devices that are commonly referred to as SSRs. Many high-power industrial SSRs, known and “hockey pucks”, are actually optically isolated TRIACs. These can range from devices that have load current ratings of a few hundred milliamps to hundreds of amps. For strictly AC environments, thyristor devices still enjoy a wide acceptability in many commercial and industrial applications. They offer operation at high power ranges with acceptably low on-state voltage drops.

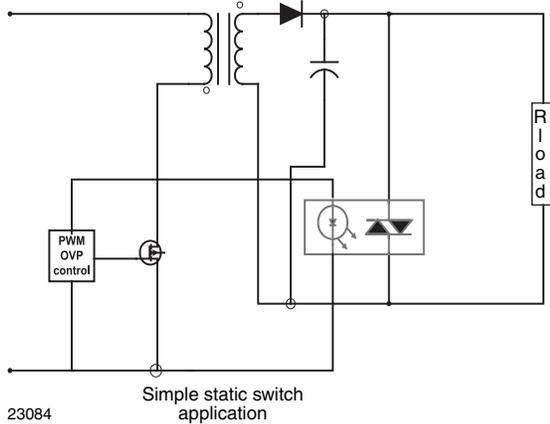


Fig. 19 - Simple Static Switch Application

An additional power supply application is the use of a TRIAC as an AC switch to bypass the inrush limiting element in a power supply. In most cases this function is accomplished by the use of a mechanical relay; however, a phototriac or phototriac/power-TRIAC combination can often perform this function with the added advantage of solid-state reliability, as illustrated in Fig. 20.

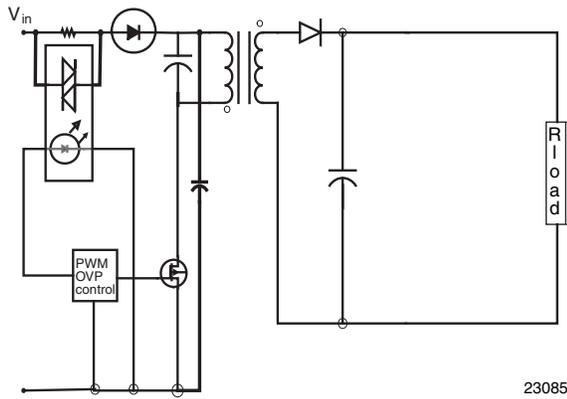


Fig. 20 - Inrush Limit Bypass Application



Fig. 21 - Commercial High-Power SSRs

Vishay offers an extremely broad range of phototriac to drive power TRIACs. Vishay’s phototriacs provide designers with flexible and economic alternative to more expensive “hockey puck” solutions (Fig. 21). Fig. 22 and Fig. 23 illustrates alternative to using a commercial solution in a high-power AC switching application. Many “hockey pucks” employ lower power phototriac drivers in their designs. If cost is a primary concern, this alternative can offer high-power performance for the price of an off-the-shelf power TRIAC and phototriac IC driver.

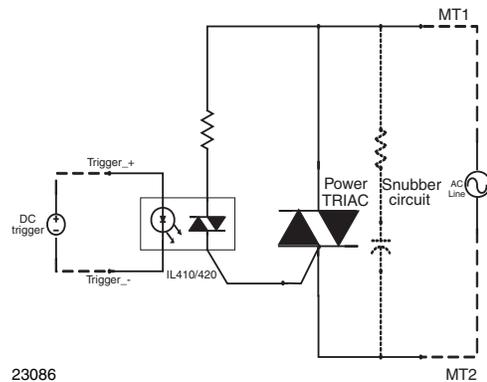


Fig. 22 - TRIAC Driver Basic SSR

Phototriac Basics

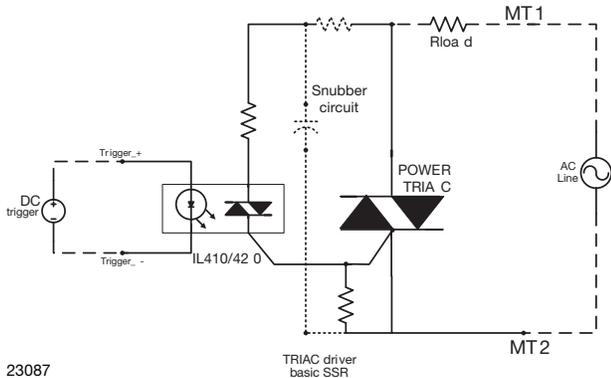


Fig. 23 - TRIAC Driver Basic SSR

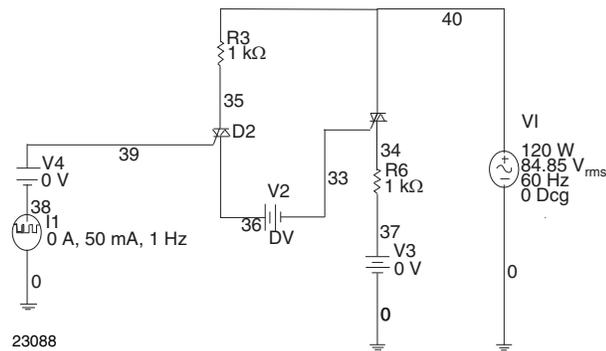


Fig. 24 - In Depth TRIAC Driver Model

In applications where a phototriac works as a power TRIAC driver, commutating dv/dt is less of an issue when a narrow pulse is used to trigger the power TRIAC than when a phototriac is used to drive a load directly. This is because in the case of a driver circuit the phototriac immediately turns off when the main TRIAC turns on; therefore the driver phototriac has an entire half-cycle in which to discharge its gate charge. This concept is illustrated in Fig. 25.

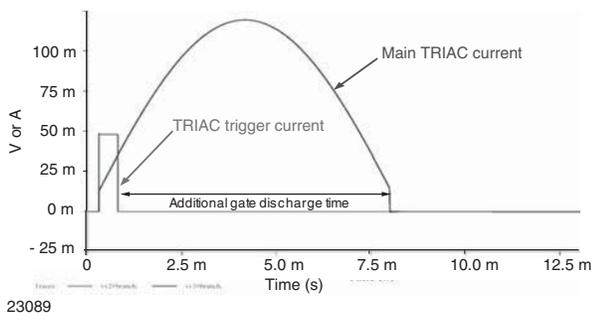


Fig. 25 - TRIAC Driver Waveforms

CRITICAL DESIGN PARAMETERS

The critical design parameters to be considered for phototriacs are its DC, AC, and thermal characteristics.

DC CHARACTERISTICS

From a designer's point of view understanding the key parametric characteristics of a phototriac is very similar to understanding an ordinary TRIAC. The main difference rests with the way in which the trigger current is supplied to the TRIAC. Unlike a standard TRIAC, where the trigger current is supplied directly, the trigger current for a phototriac is supplied indirectly by means of a photocurrent generator on the detector side; however, the designer can treat this current just the same as the trigger current for any standard TRIAC. This has to be qualified with the caveat that when calculating the worst case I_{FT} , one has to go through a worst case analysis similar to that described in the beginning section of this document.

The next crucial parameters to be considered are V_{DRM} and $V_{D(RMS)}$. These parameters describe what is commonly referred to in the TRIAC world as the breakover voltage. In Vishay's datasheets, these two parameters are referred to respectively as off-state-voltage and repetitive peak off-state-voltage. It describes the maximum voltage that can be placed across the anode-cathode terminals of a phototriac, without "turning on" the device. In some Thyristor devices, such as DIACs, this is the normal operating mode; however, when it comes to phototriacs and photoSCRs, this maximum voltage value should never be exceeded to avoid permanent damage to the part.

In conjunction with the off-state-voltage and repetitive peak off-state-voltage, it is sometimes necessary to take into account the off-state-current $I_{D(RMS)}$. This parameter denotes the phototriac's leakage-current, or the current that the device will pass in its off-state. An occasion where this may be critical is when a phototriac is being used as a triac driver and driving a triac with a particularly low trigger current. In its continuous operating region, it is also important to know what the expected voltage across the device will be, when the device is turned on. This parameter is referred to as the on-state voltage or V_{TM} . This parameter in conjunction with the on-state-current I_{TM} is most often used to determine the maximum operating point of the device at any particular ambient temperature.

Thyristors are latching devices, when used in DC mode. That is to say that, once triggered they will conduct even if the triggering signal is henceforth removed. These devices are turned off by lowering the current through the device to a very low value, close to zero. Exactly how much current through the TRIAC is required to keep it in conduction mode is referred to as holding-current or I_H .

Most of the important DC characteristics that must be considered when designing with phototriacs can be graphically measured using a standard curve tracer. This instrument will produce a set of curves such as the one in Fig. 26.

Phototriac Basics

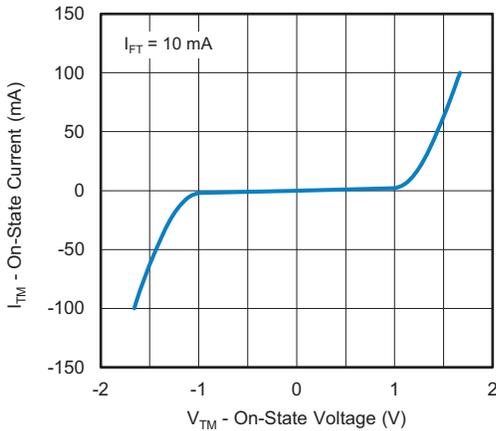


Fig. 26 - Characteristics Curve of an Phototriac

AC CHARACTERISTICS

In addition to the DC characteristics that need to be considered when designing with phototriacs, there are some very important AC characteristics that need to be considered. One of the most important of these is the dv/dt of the output waveform. The output dv/dt parameters can be divided into two separate categories, and which of these we consider depends on the state of I_F . If I_F is continuously off, dv/dt_{crq} (static dv/dt) becomes the parameter of interest. While if I_F is changing, dv/dt_{cr} (commutating dv/dt) is the parameter that should be examined. The differences between these two dv/dt parameters are graphically explained in Fig. 27.

When using TRIACS, inductive loads present a problem because the voltage and current are not in phase with each other. Since the TRIAC turns off at zero current, it may be trying to turn off when the current is zero but the applied voltage is high. To a TRIAC, this appears like a sudden rise in applied voltage, which would turn on the TRIAC if the rate of rise exceeds the device commutating dv/dt_{cr} .

If and when the transient voltage disturbance on the AC line is higher than the rated static dv/dt of the TRIAC, the TRIAC will be triggered on. This is usually not a big problem because the TRIAC will turn off at the next zero crossing of the line voltage, and most loads are not noticeably affected by an occasional single half cycle of applied power. Thus whether or not dv/dt_{crq} is important depends on the user's application.

In either case of output voltage dv/dt , it is important to note that Vishay has phototriacs available with the **highest dv/dt** ratings available in the industry. Some of these can go as high as 10000 V/ μ s. Having such high dv/dt ratings allows for the design of TRIAC circuits that can handle very rapidly changing output voltages without the need for snubber circuits. This inherent dv/dt immunity, reduces parts count, inefficiency, circuit size, and overall cost.

Getting an idea of how fast your load voltage changes is simple in the case of a sinusoidal output waveform. When the dv/dt waveform is a more complex function such as a transient produced by the "inductive kick-back" of a highly inductive load, a measurement is worth a thousand impressive calculations. In the simple case of a sinusoidal output waveform, the analysis would flow as follows:

$$V = V_{peak} \sin(\omega t)$$

$$dv/dt = V_{peak} \cdot \omega \cdot \cos(\omega t)$$


given $\rightarrow V_{peak} = \dots \cdot V_{rms}$

-
-
-

$$dv/dt = 8.89 \cdot V_{rms} \cdot f$$

where f = frequency.

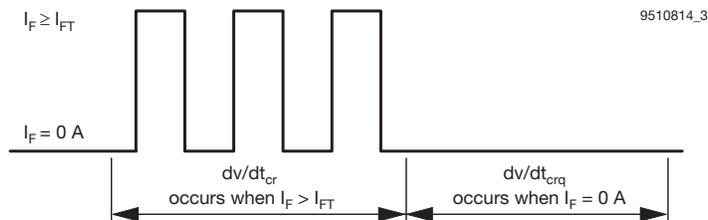For additional information on TRIAC AC characteristics, specifically TRIAC output dv/dt concerns and considerations refer to "TRIAC dv/dt Application Note" (www.vishay.com/doc?84791).



dv/dt_{cr} Highest value of the "rate of rise of off-state voltage" which does not cause any switching from the off-state to the on-state

dv/dt_{crq} Highest value of the "rate of rise of commutating voltage" which does not switch on the device again, after the voltage has decreased to zero and the trigger current is switched from I_{FT} to zero

Fig. 27 - dv/dt_{cr} and dv/dt_{crq}

Phototriac Basics

PHASE MODULATION CONTROL

While zero-voltage crossing is desirable from an RF noise generation point of view, it is not possible for many AC switching applications. In general, when the switching time constants of the physical control phenomena involved are close to or less than the half cycle of the line voltage, zero-voltage switching is not effective because the control resolution is too rough.

For example if one is trying to control a light-bulb's output intensity, it is desirable to have continuous resolution over the entire range of operation. With zero-voltage switching, the smallest increment that could be achieved in terms of control resolution would be one half of the line frequency period. In the case of heater control, the time constant of the thermal phenomena to be controlled is so large that one half cycle of line voltage resolution would be adequate in most cases.

Applications that require a finer control resolution than is achievable with zero-voltage control can be met by using a technique known as phase modulation (PM) control. This technique requires the TRIAC to be fired anywhere along the line voltage conduction angle, with the operating principle being that the conduction angle is varied to increase or reduce the resulting overall RMS voltage at the output, as illustrated in Fig. 28 and Fig. 29. The disadvantage of this technique is that there is an inherent increase in the level of RF that is generated. When fine resolution is required, however, this is a price that must be paid with greater effort being expended to achieve a low-EMI PCB layout, filtering, and, as a last resort, shielding.

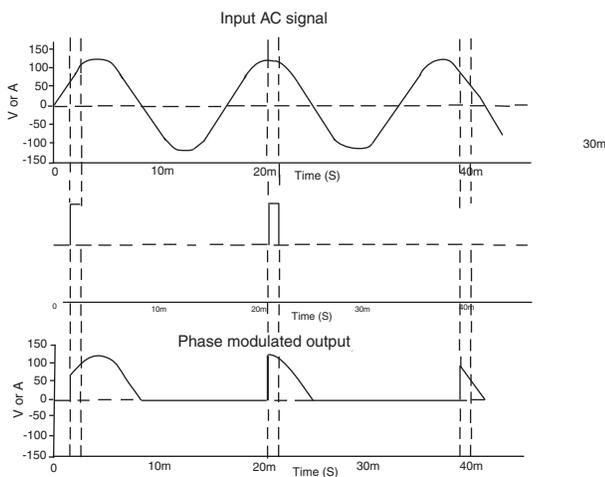


Fig. 28 - Phase Modulation Control

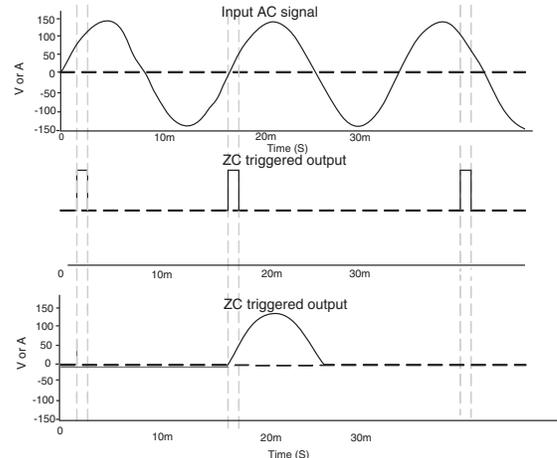


Fig. 29 - Zero-Crossing Modulation Control

All applications that require fine resolution control are good candidates for PM control and can utilize the NZC family of phototriacs. Examples of applications requiring this type of solution would be lighting dimmers, universal motor controls where continuous speed control is required, SCR-based voltage regulators, and SCR-based welders. In all these examples, zero-voltage crossing would result in too coarse a solution in terms of output voltage control. An excellent choice for the ZC application would be the IL420 product family (www.vishay.com/ppg?83629, www.vishay.com/ppg?83630) because it has the superior performance of the IL410 product family (www.vishay.com/ppg?83627, www.vishay.com/ppg?83628) but allows for NZC operation.

THERMAL DESIGN PARAMETERS

The last set of parameters that should be considered are the thermal design parameters. Vishay phototriacs are designed to operate at power dissipation levels as high as 0.5 W. When one is dealing with a DIP-6 package, this is “not” an insignificant amount of power. Moreover, TRIACs are often used in applications where the ambient temperature is other than standard room-temperature. Such is the case in many industrial and process control applications.

There are different approaches to take in the case of thermal design. The first is to go simply by a component derating number given in (power/degrees). This is the simplest and safest approach to take. Manufacturers are very conservative when deriving this number. Consequently, if a designer follows this criteria it is unlikely that he will get in trouble. The second approach is very similar to this, but instead of a simple number, the designer follows a graph of allowable power vs. temperature similar to the one in Fig. 30. Again, this is a very conservative approach and should allow for a very reliable design.

Phototriac Basics

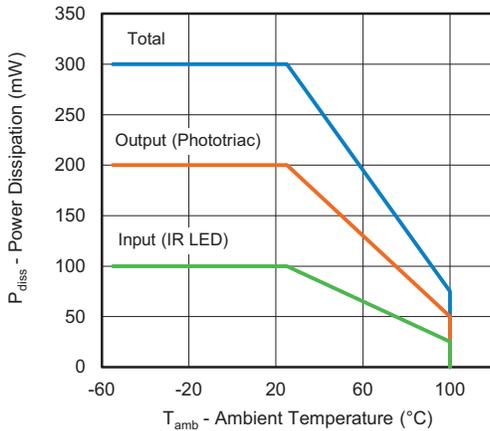


Fig. 30 - Allowable Dissipated Power

If the above two methods are not sufficient for the application, it is possible to calculate the thermal operating conditions, based on the given thermal impedance data, where such data is available.

The fundamental formula to remember when performing thermal resistance is the following:

$$\theta_j = \Delta T / \Delta P_{dis}$$

P_{dis} is in watts while ΔT can either be in Celsius or Kelvin. Since relative and not absolute temperature quantities are involved Celsius or Kelvin can be used.


If someone requires convincing, they should try it both ways. The result will be the same.

The previous method “is” quite straight forward and simple, the complication comes in getting the appropriate θ_{jx} .

One can have the following forms of θ_{jx} , θ_{jc} (junction-to-case), θ_{jb} (junction-to-board), θ_{jj} (junction-to-junction, as can be found in hybrid circuits such as optocouplers), and θ_{ja} (junction-to-ambient). As is the case for most low power IC manufacturers, Vishay usually gives the θ_{ja} values for most parts. In some occasions θ_{ja} values are given for the LED and detector. In such cases, the conservative approach is to calculate both separately, and take the worst case.

It is important to note that published junction temperatures are “absolute” maximums. They should not be designed to or even approached if at all possible. It is an established fact that reliability and operating temperature are closely linked and inversely proportional when dealing with semiconductor devices.

SAMPLE CIRCUITS

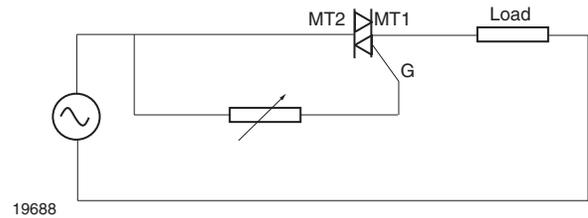

19688

Fig. 31 - Phase-Shift Controller

Fig. 31, in spite of its apparent simplicity, forms the basis of a great deal of practical TRIAC circuits. It is sometimes referred to as a “phase-shift controller”. If the input to the above circuit is a sinusoidal waveform, the output will be some “chopped up” fraction of that waveform. This allows for the efficient and economical control of the rms AC voltage. Some variant of this type of control is often used in commercial/consumer applications such as light-dimmers, and universal motors.

Vishay’s phototriacs can handle currents in the range of 100’s of mA. However, many TRIAC applications require current handling capability of several amps. In such applications, discrete phototriacs can not be used directly, but can be used in conjunction with standard high power TRIACs to yield simple, low partcount, cost effective solutions to higher power AC switching applications. In this type of application, phototriacs are used as “TRIAC drivers”. In other words, they provide the gate current and isolation required to drive standard high power TRIACs, as seen in the drawing on the right-hand top of this page.

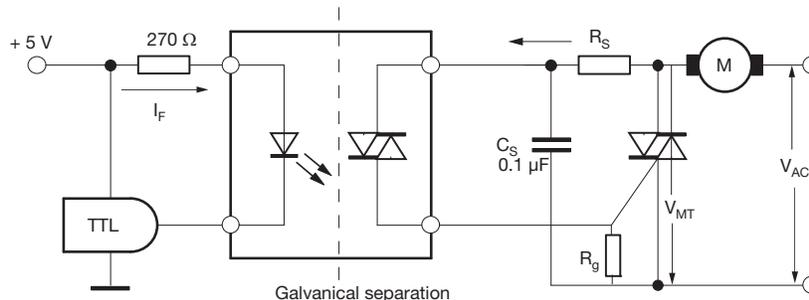


Fig. 32 - TRIAC Driver Example

Phototriac Basics

In addition to providing an example of an application where a phototriac is used as a TRIAC driver, the above circuit illustrates the concept of using a snubber circuit and one of the main advantages of Vishay’s phototriacs.

The circuit in Fig. 32 is driving an electric motor, which under most circumstances is a highly inductive load. This in turn leads to unique difficulties in terms of output dv/dt. When inductive loads are switched rapidly they generate high transient spikes quantified by $V = L \times di/dt$. The L in the case of even small electric motors is comparatively large, thereby generating equivalently large values of dv/dt on the output. Such large skewing in output voltage could generate false triggering as described in previous sections.

There are two options to deal with this problem. The first is to use Vishay’s high dv/dt (10000 V/μs) phototriacs, because the high dv/dt will solve the problem.

The second is to add a snubber similar to the one included in the circuit shown above.

The basic design process for arriving at the most advantageous snubber possible is as follows:

1. What is the highest tolerable dv/dt that a particular phototriac can withstand?
2. Use $dv/dt = V/(R_s \times C_s)$ to come up with an appropriate RC combination

In addition to having the highest dV/dt specifications in the industry, Vishay optocouplers are also available with internal zero crossing features. This is to say that for the ZC phototriacs, they are designed such that they can be triggered only when the load voltage is nominally at zero volts. Incorporating this feature in various applications greatly decreases circuit complexity and reliability, by reducing the number of parts required to implement this functionality.

As in the case for optocouplers in general, phototriacs are well suited for the current trend towards increasing embedded intelligence and microprocessor control. By allowing the designer to separate the “powerstage” from the low power controller stage of the system it allows for simpler and lower cost designs. This is true in industrial automation where microprocessor based systems control large numbers of widely varying AC and DC loads.

In addition to Industrial process controls, there is an increasing trend to the use of solid-state switches, to replace traditional EMRs (Electro Mechanical Relays) in the consumer appliance market. Solid-state switches such as TRIACs and SSRs offer highly reliable solutions that are well suited to the increasingly microcontroller dominated consumer market place.

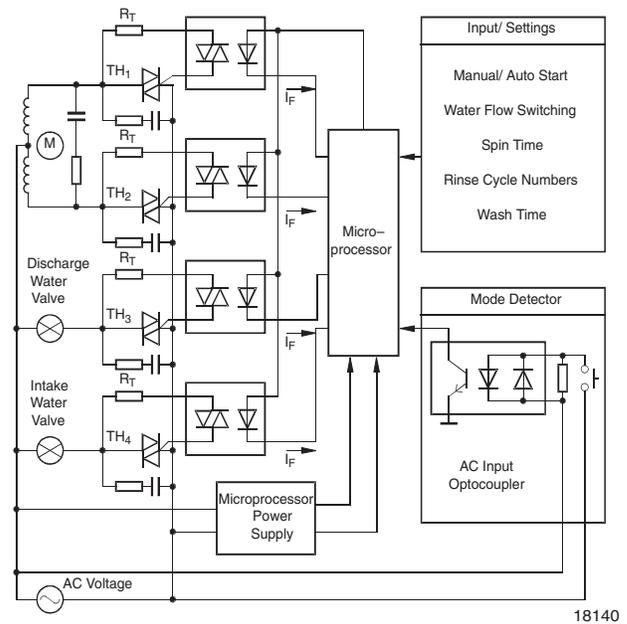


Fig. 33 - Consumer Appliance Example

18140

Phototriac Basics

MICROWAVE OVEN WITH GRILL

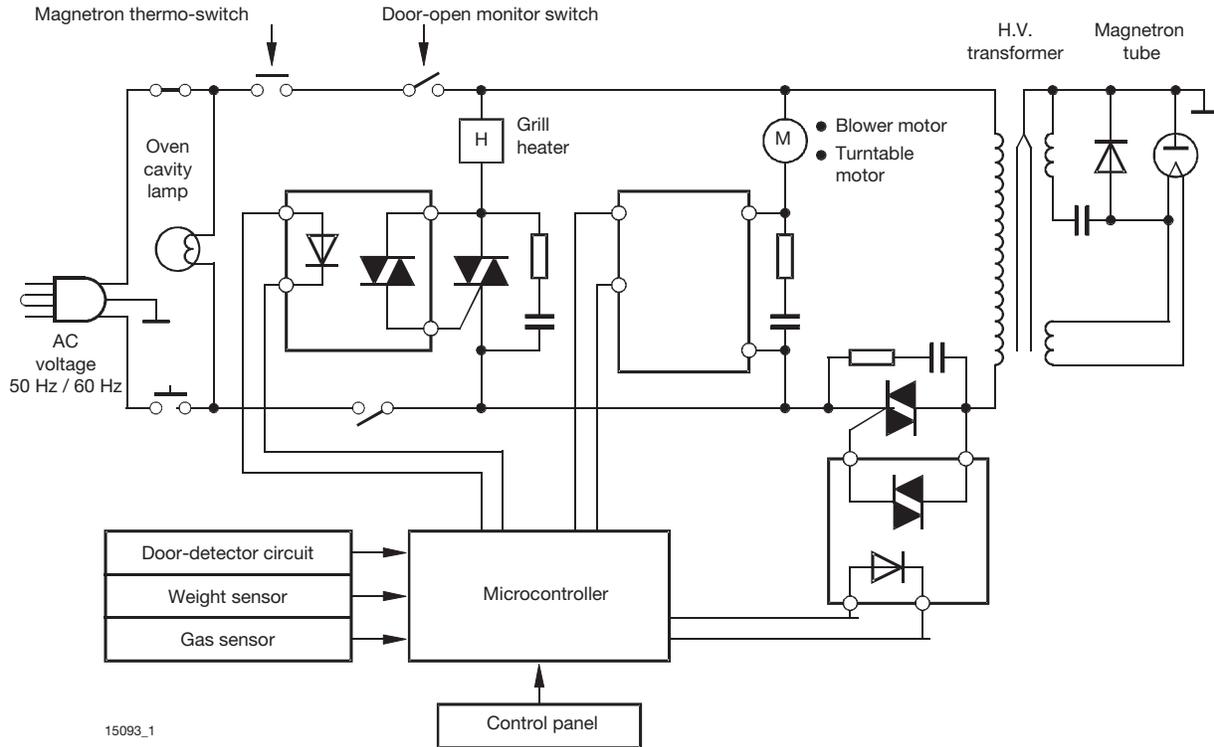


Fig. 34 - Microwave Oven With Grill Example

References:

Herman L. Stephen, Industrial Motor Control. Albany, NY: Delmar Publisher, 1998.

Malvino Albert Paul, Electronic Principles, NY, McGraw Hill, 1983.

Mazur Glen & Rockis Gary, Electrical Motor Controls, Homewood Ill., American Technical Publishers Inc., 1997.