



# AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

by Ronald Vinsant

## ABSTRACT

There are many applications that require that a voltage rail within a system be capable of being adjusted by a digital or analog control signal. These circuits may only need to do a margining function in a test mode, vary the output voltage from the regulator by only a small amount to optimize specific performance parameters, or perhaps the voltage must be widely scalable to allow for the use of different sensors in an industrial application. This application note will show a number of different solutions to these design challenges by utilizing the Vishay SiC40X series of synchronous buck regulators. A key aspect of this design is the COT architecture of this family of products, which allows adaptability of the control system to the different operating points of the regulator without any iterative compensation design.

A spreadsheet tool and simulation schematic will be introduced that enable the user to quickly derive a solution with knowledge of only a few required parameters. Confirmation of the validity of these two tools will be shown by use of the SiC401DB, SiC402DB, and SiC403DB reference board, with the addition of only two resistors, a capacitor, and a user-supplied voltage source. This source could be an existing rail with an analog switch, a GPIO or PWM on an FPGA or processor, or a DAC.

## SiC40X DESCRIPTION

The Vishay Siliconix SiC401A/B, SiC402A/B, and SiC403A/B are advanced stand-alone synchronous buck regulators, featuring integrated power MOSFETs, a bootstrap switch, and a programmable LDO in space-saving PowerPAK® MLP55-32L pin packages.

The SiC401A/B, SiC402A/B, and SiC403A/B are capable of operating with all ceramic solutions and switching frequencies up to 1 MHz. The programmable frequency, synchronous operation, and selectable power-save feature allow operation at high efficiency across the full range of load current. See [www.vishay.com/doc?62768](http://www.vishay.com/doc?62768).

## THE REFERENCE BOARD

This reference board allows the end user to evaluate the SiC401A/B, SiC402A/B, and SiC403A/B for their features and all functionalities. It can also be a reference design for a user's application. See [www.vishay.com/doc?62923](http://www.vishay.com/doc?62923).

## CALCULATION TOOLS

The designer can start their design by using the reference board mentioned above. If the reference board does not meet the goals of the designer's application, then a design tool is available online at [www.vishay.com/doc?62923](http://www.vishay.com/doc?62923).

Once a regulator design has been chosen, there is an Excel tool, an AVS calculator, located at [www.vishay.com/doc?77389](http://www.vishay.com/doc?77389).

This tool allows the designer to add to the existing regulator circuit adjustability of the output voltage through an external signal from a DAC or other voltage source. In addition, this spreadsheet has some programmer's tools to make the writing of software to drive the DAC easier.

# AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

## HOW IT WORKS

### Theory

To describe the theory of operation, a design from Vishay's AVS calculator tool has been chosen that extends to the boundaries of operation of the SiC40X family of regulators (Fig. 1). The yellow cells indicate the only parameters required from a user to generate a design. Details of the calculator will be covered later in this application note.

Step 1: Calculate $R_{TOP}$ and $R_{DAC}$									
$V_{REF}$ (V)	$R_{BOT}$ (R23 above) ( $\Omega$ )	$I_{RBOT}$ (A)	SiC4XX $V_{OUT}$ max. (V)	SiC4XX $V_{OUT}$ min. (V)	Determine DAC gain (DAC V / output V) (ratio)	Determine zero $R_{DAC}$ current point for $V_{OUT}$ ( $V_{DAC} = V_{REF}$ ) (V)	Calculate $R_{TOP}$ ( $\Omega$ )	Calculate $R_{DAC}$ ( $\Omega$ )	
0.6	5110	0.000117	5	0.25	-1.9	3.86	27764.33	14612.81	
Step 2: Input DAC parameters									
DAC max. $V_{OUT}$ (V)	DAC bits (number)	DAC LSB (V)	1 DAC LSB adjust in SiC4XX $V_{OUT}$ (V)	Total count (theoretical number of voltage steps from DAC) (number)					
2.5	16	$3.81^{-5}$	$7.24792^{-5}$	65536					

Fig. 1 - Calculation Results for Theory of Operation

Fig. 2 shows a schematic of the reference board. The area circled in black is where a signal will be injected to alter the output voltage. R53, R54, and C38 have been added to the original schematic. In all the simulations below, the op-amps that are used are very close to ideal, thus the calculations are very exacting.

 


Fig. 2 - Reference Board Schematic (Modified)

The circled area in Fig. 2 provides a simplified view of DC operation.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 3 - Operation at “Zero R<sub>DAC</sub> Current Point”

In Fig. 3 it can be observed that the SiC40X control loop will maintain the reference voltage, V<sub>2</sub>, at “FB, pin 1” under normal operation. It can be assumed then that the current in R<sub>23</sub>, R<sub>BOT</sub>, will always be 117 μA. It can be further observed using Kirchhoff’s Current Law that the sum of the currents at node 4 from R<sub>DAC</sub> and R<sub>TOP</sub> must be equal to the current in R<sub>BOT</sub>. The case shown in Fig. 3 is the “zero R<sub>DAC</sub> current point” from the calculator in Fig. 1, where the voltage at probe 4, node 8 is equal to the voltage at probe 2, node 4. At this operating point, all current to R<sub>BOT</sub> has to be supplied by R<sub>TOP</sub>. The DAC has no effect on V<sub>OUT</sub>. Thus:  $V_{OUT} = 0.6 \times (1 + R_{10}/R_{23}) + V_{RIPPLE}/2$  (see SiC40X datasheets for further information).

Now let’s examine lowering the voltage at probe 4, V<sub>DAC</sub>.


 


Fig. 4 - Operation at V<sub>DAC</sub> Lower than V<sub>REF</sub>

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

As the DAC voltage is changed below the reference voltage ( $V_{REF}$  at node 6 in Fig. 4), the current through  $R_{DAC}$ ,  $R_3$ , goes negative. To make up for current being drawn out of node 4, the output voltage has had to rise so that there is more current from  $R_{TOP}$  to make up for the current drawn out through  $R_{DAC}$ , as can be observed in probes 2, 4, and 3. Notice that the voltage across  $R_{BOT}$ ,  $R_{23}$ , is still 0.6 V, thus the current in  $R_{23}$  is constant at 117  $\mu$ A.

The next step is to raise the voltage at probe 4,  $V_{DAC}$ .

 

**Fig. 5 - Operation at  $V_{DAC}$  Higher than  $V_{REF}$**

Fig. 5 simulates a rise in the DAC voltage above  $V_{REF}$ , node 6, and the current through  $R_{DAC}$ ,  $R_3$ , has gone positive. To make up for this current being forced into node 4, the output voltage has had to fall so that current has to be pulled out of node 4 through  $R_{TOP}$  to make up for the current being sourced through  $R_{DAC}$ , as can be observed in probes 2, 3, and 4. Notice that the voltage across  $R_{BOT}$ ,  $R_{23}$ , is still 0.6 V, thus the current is constant at 117  $\mu$ A. In this case  $V_{OUT}$  from the SiC40X is actually below  $V_{REF}$ ,  $V_2$ .

### CONTROL LIMITS OF $V_{OUT}$

There is a sacrifice in performance that is made though when  $V_{OUT}$  goes too far below  $V_{REF}$  and the current from  $R_{DAC}$  becomes positive; as this current forces  $V_{OUT}$  lower, the effective open loop gain of the regulator declines. Put simply, the output voltage regulation gets worse. This is due to the inability of the SiC40X control system to work close to a zero duty cycle and its circuitry to operate near to or at zero volts.

The values shown in the circuit in Fig. 5 were used in the reference board in Fig. 2, which was constructed and tested for output voltage regulation at three operating points: 5 V (Fig. 6), 0.25 V, and the “zero  $R_{DAC}$  current point” of 3.9 V with a fixed 12 V input to demonstrate this point.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 6 - 5 V Output Load Regulation

 


Fig. 7 - 3.9 V Output Load Regulation

 


Fig. 8 - 0.25 V Output Load Regulation


### AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

There is no difference in the regulation of the 5 V and 3.9 V outputs, but the 0.25 V output regulation is substantially worse, as expected. Practical limits for wide output range designs are from 1.5 V to 5 V for reasonable output regulation. See circuit 3 as an example.

Key point: Optimal performance occurs with  $V_{OUT}$  at levels from 1.5 V to 5 V.

#### ADDITIONAL DESIGN CONSIDERATIONS

Besides the obvious error terms of resistor and  $V_{REF}$  tolerance (see “How to Obtain Exacting Resistor Values”), there are a number of other issues that can affect the output voltage tolerance. Let’s look at the boundary conditions of the control system.

 

**Fig. 9 - DAC Limitation at Zero Volt Output**

If  $V_{DAC}$  is brought to zero volts, as in Fig. 9,  $V_{DAC}$ , probe 4 is at 57.8 mV, not zero. That is due to the inability of most DACs to actually get to zero volts, even “rail-to-rail” designs.

Key point: these designs are based on an “ideal” voltage source.

Allowances may need to be made for deviations from the ideal.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 10 - Addition of Negative Rail to DAC Buffer

In Fig. 10 a negative voltage, V5, is added to the DAC circuit and now the output of the DAC simulation at node 8 actually goes to zero volts and the regulator output voltage matches that of the calculator spreadsheet. A DAC with a buffer can have a negative supply to allow V<sub>DAC</sub> to go to zero.

Key point: watch for non-linearity in the DAC (voltage source), both at the lower and upper ends of its output range.


 


Fig. 11 - Simulation Showing Effect of Input Bias Currents

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

If there is an input current required on the “FB, (pin 1),” then this current will subtract from  $R_{BOT}$ , R23. In the simulation in Fig. 11, R1, a 500 k $\Omega$  resistor, was added from “FB, (pin 1)” to ground. This requires that an additional 1.2  $\mu$ A be supplied by  $R_{TOP}$  so the output voltage, observed at probe 3, rises by 33 mV to add the required current to keep node 4 at 0.6 V.

Key point: watch for input offset currents.

 

**Fig. 12 - Effect on  $V_{OUT}$  Setting Due to Influence of Ripple**

Referring to Fig. 12, let us look at the effects of ripple on  $V_{OUT}$ . Since most switching regulators have some output ripple, one has to consider that this is a noise component whose average value can affect the feedback of the regulator.

Referring back to Fig. 5, it can be seen that when we set the DAC voltage in our simulation of this design to 2.3684 V (shown as 2.37 V at probe 4), we get an output of 500.09 mV.

If we then add a 20 mV peak-to-peak 500 kHz “ripple” to the output and R1 (as shown in Fig. 11) is removed so that the offset current will not influence the result, we can observe the effect of the injected ripple signal.

The output voltage has dropped about 2 mV, demonstrating that ripple and noise can affect  $V_{OUT}$  also. In an actual application where the bandwidth of the control loop is less than the op-amps in the simulation model, the effect will be greater; typical values are 5 mV to 10 mV.

### CALCULATOR

The calculator requires that users know five different parameters:

1.  $V_{REF}$
2.  $R_{BOT}$
3. SiC40X output voltage range (the minimum voltage and the maximum voltage)
4. The maximum output voltage of the DAC
5. The number of DAC bits

All other parameters are calculated for users.

There is a section that is useful for programmers that allows the translation of DAC counts in decimal and hex format to  $V_{OUT}$  and  $V_{DAC}$ .

### AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

#### EXAMPLE DESIGNS

##### Circuit 1: AVS Design

This is a circuit that would be useful to most AVS and margining applications that are in the 1 V region. Fig. 13 shows the results from the spreadsheet design tool.

Step 1: Calculate $R_{TOP}$ and $R_{DAC}$									
$V_{REF}$ (V)	$R_{BOT}$ (R23 above) ( $\Omega$ )	$I_{RBOT}$ (A)	SiC4XX $V_{OUT}$ max. (V)	SiC4XX $V_{OUT}$ min. (V)	Determine DAC gain (DAC V / output V) (ratio)	Determine zero $R_{DAC}$ current point for $V_{OUT}$ ( $V_{DAC} = V_{REF}$ ) (V)	Calculated $R_{TOP}$ ( $\Omega$ )	Calculated $R_{DAC}$ ( $\Omega$ )	$R_{DAC}/2$ ( $\Omega$ )
2.5	5110	0.000489237	3.4	3.1	-0.12	3.1	1226.4	10 220	5110
Step 2: Input DAC or voltage source parameters									
DAC max. $V_{OUT}$ (V)	DAC bits (number)	DAC LSB (V)	1 DAC LSB adjust in SiC4XX $V_{OUT}$ (V)	Total count (theoretical number of voltage steps) (number)					
2.5	12	0.000610352	$7.32422 \cdot 10^{-5}$	4096					

Fig. 13 - Design Tool Calculations for Circuit 1

 


Fig. 14 - Simulation Schematic (Refer to Fig. 2 for Actual Schematic)

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

### Shaping $V_{OUT}$ Response

Fig. 2 shows how  $R_{DAC}$  has been cut in half so that there are two resistors, R53 and R54, allowing a capacitor to be added in between them. This capacitor will shape the response of  $V_{OUT}$  to a transition command from the  $V_{DAC}$ .

If the response time,  $t_r$ , is set at five time constants so it is close to 20  $\mu$ s, this will result in the best response time of the regulator. This time can be determined from:

$$t_r = 1/(f_{sw} \times 0.1) \text{ and } t_r = (R_{total}) \times C38 \times 5,$$


where:  $R_{total} = R54 \parallel R53$  for  $f_{sw} = 500$  kHz, then:

$$1/(0.1 \times 500\,000) = 20 \times 10^{-6} \text{ s, or } 20 \mu\text{s. Divide by five and something close to } 5 \mu\text{s is required.}$$

Since R54 has been set equal to R53, then  $R54 \parallel R53 = 0.5 \times R53$  or 12 k $\Omega$ . Thus:


$$12 \text{ k}\Omega \times 470 \text{ pF} = 5.64 \mu\text{s} \times 5 \text{ is } 28.2 \mu\text{s. } 470 \text{ pF was chosen as it is a standard value.}$$

In a simulator it looks like this, where the reference values (R54, C38, and R53) refer to Fig. 2:

 

**Fig. 15 - Transient Simulation Circuit**

These are the simulation results.

 

**Fig. 16 - Transient Step Simulation Result**

(Note: V1 and V2 Refer to the Voltages at the Nodes 1 and 2, not to the Sources V1 and V2)

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

Here is what the output voltage transition of the regulator looks like (showing a 10 % to 90 % rise time):

 


Fig. 17 -  $V_{OUT}$  Transition at no Load

Referring to Fig. 2, channel 1 is a regulator  $V_{OUT}$  at P10 (yellow) with 1 V offset, channel 2 is  $V_{DAC}$ , and channel 3 is the LX node at J5. Conditions are no load on  $V_{OUT}$ , 12 V input.

Here is the same transition but with a 6 A load (all scope settings the same as Fig. 17):

 


Fig. 18 -  $V_{OUT}$  Transition at 6 A Load

Key point: loading does not substantially affect the  $V_{OUT}$  transition speed.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

### Transient Response of Circuit 1

Again, referring to Fig. 2, let us look at how the COT architecture of the SiC40X results in a fast response to both load and  $V_{DAC}$  commands.



Fig. 19 - Increasing Transient Load with Static DAC Setting



Fig. 20 - Load Release with Static DAC Setting

Whenever two parameters change at one time, there might be unwanted effects. Let us look at what happens when both  $V_{OUT}$  and load current are changed together.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 21 - Increasing Load from 2 A to 6 A,  $V_{OUT}$  Increase from 0.95 V to 1.05 V Driven by a DAC

Let us examine the extremes; where  $V_{DAC}$  is driven from a function generator so that the  $V_{DAC}$  transition is 30 ns.

 


Fig. 22 -  $I_{OUT}$  Changes from 6 A to 2 A while  $V_{OUT}$  is Adjusted from 1.1 V to 0.96 V

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 23 -  $I_{OUT}$  Changes from 6 A to 2 A while  $V_{OUT}$  is Adjusted from 0.96 V to 1.1 V



Fig. 24 -  $I_{OUT}$  Changes from 2 A to 6 A while  $V_{OUT}$  is Adjusted from 1.1 V to 0.96 V

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 


Fig. 25 -  $I_{OUT}$  Changes from 2 A to 6 A while  $V_{OUT}$  is Adjusted from 0.96 V to 1.10 V

Excellent transient performance is observed even under the worst case conditions due to the COT architecture of the SiC403A.

### DC Load Regulation of Circuit 1


 


Fig. 26 - 0.9 V Load Regulation

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 

**Fig. 27 - 1.1 V Load Regulation**

### Circuit 2: Using a Tri-State Buffer for a Voltage Margining Circuit

With a slight modification to circuit 1, a tri-state buffer can be used in place of the DAC as a three-output voltage source;  $V_{OUT}$  is selected by the state of the buffer. For purposes of the calculator, the buffer is a “0” bit DAC.

Step 1: Calculate $R_{TOP}$ and $R_{DAC}$									
$V_{REF}$ (V)	$R_{BOT}$ (R23 above) ( $\Omega$ )	$I_{RBOT}$ (A)	SiC4XX $V_{OUT}$ max. (V)	SiC4XX $V_{OUT}$ min. (V)	Determine DAC gain (DAC V / output V) (ratio)	Determine zero $R_{DAC}$ current point for $V_{OUT} = V_{REF}$ (V)	Calculated $R_{TOP}$ ( $\Omega$ )	Calculated $R_{DAC}$ ( $\Omega$ )	$R_{DAC} / 2$ ( $\Omega$ )
0.6	5110	0.000117	1.1	0.9	-0.11111111	1.03333333	3691	33 215	16 608
Step 2: Input DAC or voltage source parameters									
DAC max. $V_{OUT}$ (V)	DAC bits (number)	DAC LSB (V)	1 DAC LSB adjust in SiC4XX $V_{OUT}$ (V)	Total count (theoretical number of voltage steps) (number)					
1.8	0	1.8	0.2	1					

**Fig. 28 - Tri-State Voltage Margining Circuit Calculation Result**

If the buffer’s output is active and is set to logic low, then there will be a 1.1 V output. If it is set at logic high, there will be a 1.1 V output. If at tri-state (not active), the  $V_{OUT}$  will be at the “zero  $R_{DAC}$  current point,” or 1.03 V output. Any tri-state output could be used from an ASIC, FPGA, etc.

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

Here are the simulations:

 


Fig. 29 - Tri-State Example with U3 at Tri-State


 


Fig. 30 - Tri-State Example with Tri-State not Active and Logic Output at Zero Volts

### AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 

**Fig. 31 - Tri-State Example with Tri-State not Active and Logic Output at 2 V**

In Fig. 31 the simulation shows a  $V_{OUT}$  of 0.877 V rather than the 0.9 V designed for. This is due to an artifact of the simulation, as the model for the buffer assumes a 2 V power rail as opposed to the intended 1.8 V rail.


#### Circuit 3: Wide Range Output

This is a wide range output example. It would be useful for a designer that needs to set the rail for output buffers at different voltages such as 1.5 V, 1.8 V, 2.5 V, 3.3 V, and 5 V.

Step 1: Calculate $R_{TOP}$ and $R_{DAC}$									
$V_{REF}$ (V)	$R_{BOT}$ (R23 above) ( $\Omega$ )	$I_{RBOT}$ (A)	SiC4XX $V_{OUT}$ max. (V)	SiC4XX $V_{OUT}$ min. (V)	Determine DAC gain (DAC V / output V) (ratio)	Determine zero $R_{DAC}$ current point for $V_{OUT}$ ( $V_{DAC} = V_{REF}$ ) (V)	Calculated $R_{TOP}$ ( $\Omega$ )	Calculated $R_{DAC}$ ( $\Omega$ )	$R_{DAC}/2$ ( $\Omega$ )
0.6	5110	0.000117	5.25	1.45	-1.52	4.338	31835	20944	10472
Step 2: Input DAC or voltage source parameters									
DAC max. $V_{OUT}$ (V)	DAC bits (number)	DAC LSB (V)	1 DAC LSB adjust in SiC4XX $V_{OUT}$ (V)	Total count (theoretical number of voltage steps from DAC) (number)					
2.5	10	0.002441	0.003710938	1024					

**Fig. 32 - Circuit 3 Calculator Result**

## AVS / DVS and Margining Circuits for Vishay Power ICs SiC40X Series SMPS Regulators

 

**Fig. 33 - 1.5 V to 5.25 V Simulation**

The calculator can be used to determine what the register settings are for the DAC. In this case, a 10-bit DAC allows a 3.7 mV per LSB adjustment of  $V_{OUT}$ .

Using the programmer's tool, the desired  $V_{OUT}$  values can be entered and the proper register values can be determined:

Convert regulator output voltage to DAC count	Regulator $V_{OUT}$	Count	Hex
	2.5	741	2E5

**Fig. 34 - Determining Register Settings for the DAC**

Using the same circuit as above, a power rail for a bridge-based sensor can also be set up. In this case bits would be added to the DAC based on calibration needs.

Input DAC or voltage source parameters			
DAC bits (number)	DAC LSB (V)	1 DAC LSB adjust in SiC4XX $V_{OUT}$ (V)	Total count (theoretical number of voltage steps from DAC) (number)
14	0.000153	0.000231934	16384

**Fig. 35 - More DAC Bits Yields Increased Resolution in  $V_{OUT}$  Adjustability**

In this circuit regulation is 1.480 V at 0 A and 1.459 V at 6 A; 5.309 V at 0 A and 5.288 V at 6 A.

