



DID YOU KNOW?


VOLTAGE DIVIDERS VS VARIABLE RESISTORS

One major difference between panel potentiometers and precision potentiometers is the way they are utilized by end users. Precision potentiometers can only be used as voltage dividers, while panel potentiometers can be used as voltage dividers and variable resistors.

Let's start with the basics. All potentiometers have three output connections. N°1 and N°3 are usually dedicated to the power supply (DC voltage) while N°2 is the wiper output, which varies in relation to the angular shaft position.

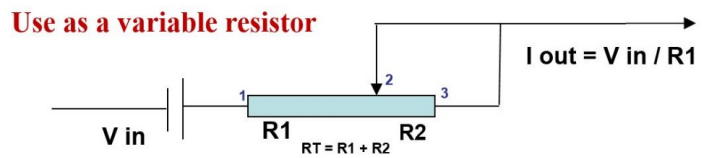1) Variable Resistor or Rheostatic Mode

For potentiometers connected as shown in the diagram to the right, a calculation must first be performed to determine if the potentiometer will support the current going through it. The signal is a current signal that depends on the wiper position and the ohmic value. The current changes accordingly to a linear variation versus ratio of ohmic value (wiper position).



Graph N°1

2) Voltage Divider


In this type of assembly, the value of the load resistance R_L is much greater than the total ohmic value of the potentiometer (frequently 1000 times greater). In this case, the output signal is a DC voltage (rather than a current signal as found in rheostatic mode). The main part of the current remains in the track, so the DC voltage V_{OUT} on the output is defined by the formula below:

$$V_{OUT} = (V_{IN} \times R_2 \cdot R_L) / (R_1 \cdot R_L + R_2 \cdot R_L + R_1 \cdot R_2).$$

As R_L is much larger than R_1 and R_2 , the formula becomes:

$$V_{OUT} = V_{IN} \times R_2 / (R_1 + R_2) = V_{IN} \times R_2 / R_T$$

(refer to graph N°2).

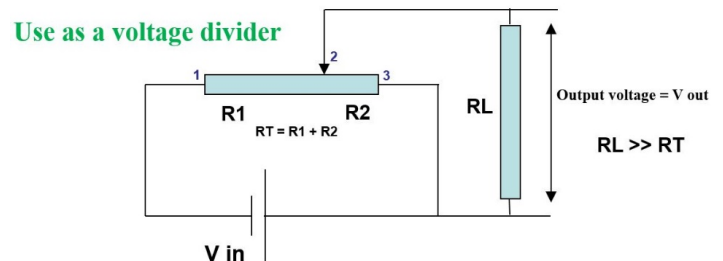

Graph N°2